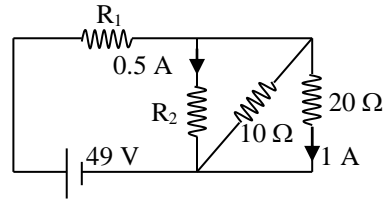


2PUC – CHAPTER 03
CURRENT ELECTRICITY

1. In the circuit shown in the given figure the resistances R_1 and R_2 are respectively
- 14Ω and 40Ω
 - 40Ω and 14Ω
 - 40Ω and 30Ω
 - 14Ω and 30Ω




2. A wire of length L and 3 identical cells of negligible internal resistances are connected in series. Due to the current, the temperature of the wire is raised by ΔT in a time t . A number N of similar cells is now connected in series with a wire of the same material and cross-section but of length $2L$. The temperature of the wire is raised by the same amount ΔT in the same time t . The value of N is
- 4
 - 6
 - 8
 - 3

3. A cell of constant emf first connected to a resistance R_1 and then connected to a resistance R_2 . If power delivered in both cases is same then the internal resistance of the cell is


- $\sqrt{R_1 R_2}$
- $\frac{\sqrt{R_1}}{\sqrt{R_2}}$
- $\frac{R_1 - R_2}{2}$
- $\frac{R_1 + R_2}{2}$

4. The plot represents the flow of current through a wire at three different times. The ratio of charges flowing through the wire at different times is

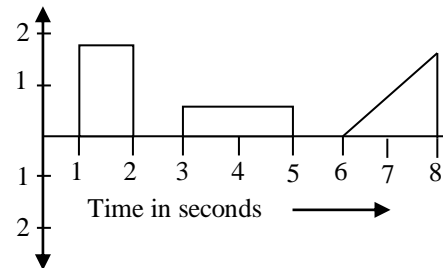- 2 : 1 : 2
- 1 : 3 : 3
- 1 : 1 : 1
- 2 : 3 : 4



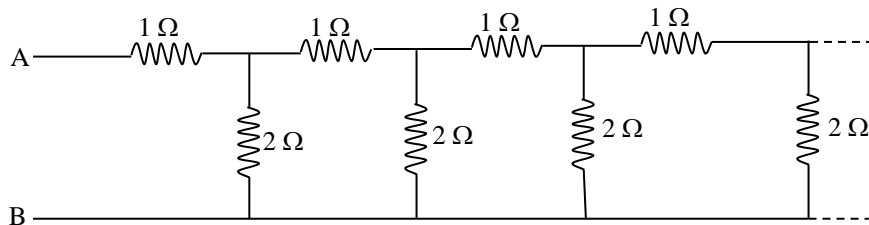5. Find the equivalent resistance of the infinite ladder between A and B.




- 1Ω
- $1 + \sqrt{5} \Omega$
- 2Ω
- $\infty \Omega$

6. The current flowing through a wire depends on time as $I = 3t^2 + 2t + 5$. The charge flowing through the cross section of the wire in time from $t = 0$ s to $t = 2$ s. Is

- 22C
- 20C
- 18C
- 5C


13. In the figure shown, the capacity of the condenser C is $2\mu\text{F}$. The current in 2Ω resistor is

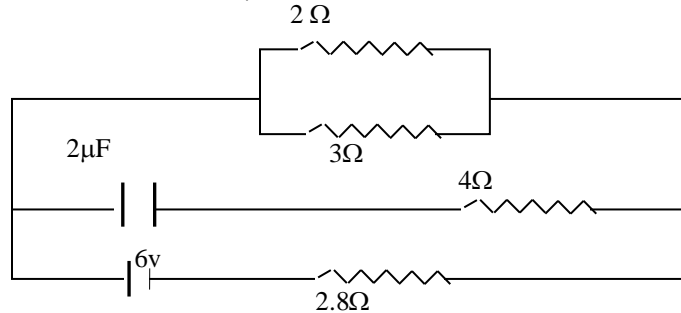- a) 9A
- b) 0.9A
- c) $\frac{1}{9}$ A
- d) $\frac{1}{0.9}$ A



14. In the shown arrangement of the experiment of the meter bridge if AC corresponding to null deflection of galvanometer is x , what would be its value if the radius of the wire AB is doubled





- a) x
- b) $x/4$
- c) $4x$
- d) $2x$

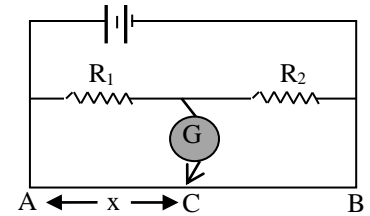

15. If voltage across a bulb rated 220 Volt-100 Watt drops by 2.5% of its rated value by which the power would decrease is


- a) 20%
- b) 2.5%
- c) 5%
- d) 10%

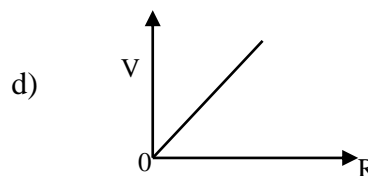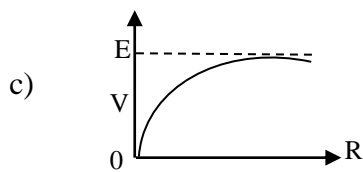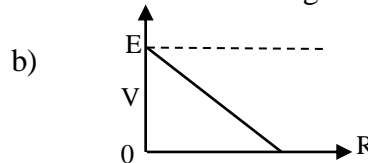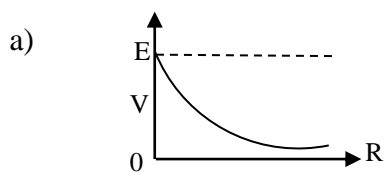16. Cell having an emf ϵ and internal resistance r is connected across a variable external resistance R . As the resistance R is increased, the plot of potential difference V across R is given by




17. The voltage V and current I graph for a conductor at two different temperatures T_1 and T_2 are shown in the figure. The relation between T_1 and T_2 is

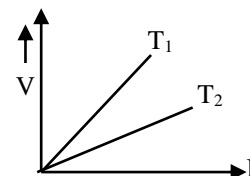- a) $T_1 > T_2$
- b) $T_1 \approx T_2$
- c) $T_1 = T_2$
- d) $T_1 < T_2$




18. A 100 W bulb B_1 and two 60 W bulbs B_2 and B_3 are connected to a 250 V source, as shown in figure. Now W_1 , W_2 and W_3 are the output powers of the bulbs B_1 , B_2 and B_3 , respectively. Then:

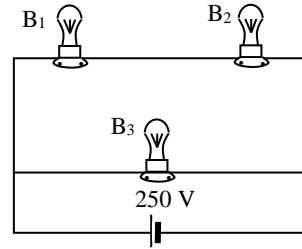- a) $W_1 > W_2 = W_3$ b) $W_1 > W_2 > W_3$
 c) $W_1 < W_2 = W_3$ d) $W_1 < W_2 < W_3$



19. If a steady current I is flowing through a cylindrical element ABC. Choose the correct relationship:

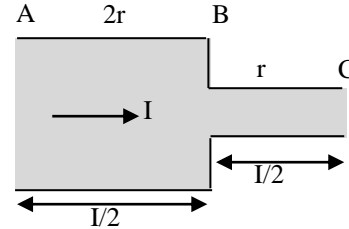
- a) $V_{AB} = 2 V_{BC}$
 b) Power across BC is 4 times the power across AB
 c) Current densities in AB and BC are equal
 d) Electric field due to current inside AB and BC are equal



20. To get maximum current in a resistance of 3 ohm, one can use n rows of m cells in each row. If the total number of cells is 24 and the internal resistance of a cell is 0.5 ohm then:


- a) $m = 12, n = 2$ b) $n = 3, m = 8$
 c) $m = 2, n = 12$ d) $m = 6, n = 4$

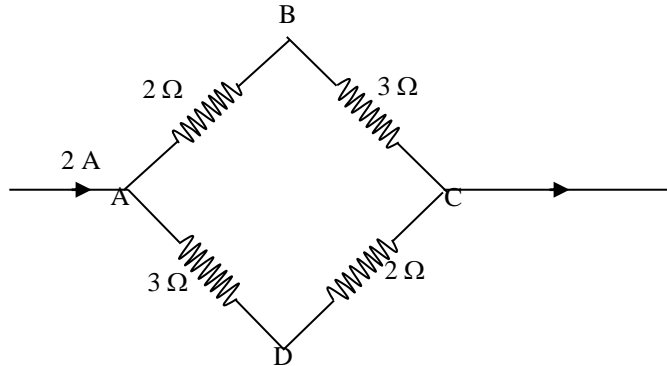21. A current of 2 A flows through the network shown in fig. The PD between points B and D is:





- a) -1 V b) +1 V c) -2 V d) +2 V

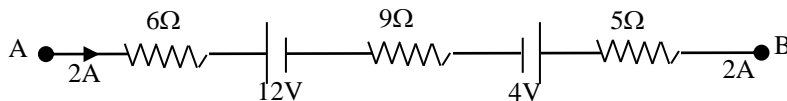22. The potential difference between A and B in the fig.




- a) 24 V b) 14 V c) 32 V d) 48 V

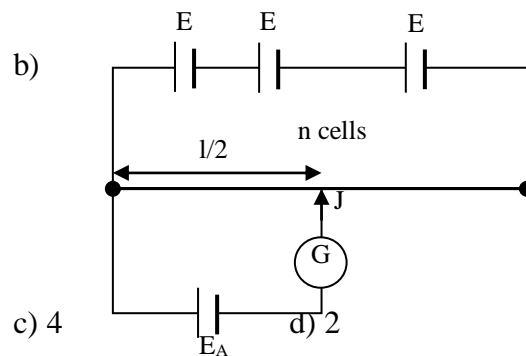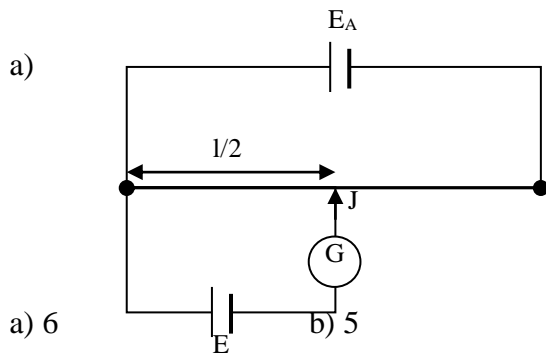29. Fig. shows a potentiometer circuit. Length of the potentiometer wire is ' ℓ '. As shown, a cell of emf E is balanced by length ' $\ell/2$ ' of the potentiometer wire. b) shows cell of emf E_A in place of E and a combination of n cells each of emf E in place of E_A . For balancing E_A at $\ell/2$, n should be



30. Consider a thin square sheet of side L and thickness t , made of a material of resistivity ρ . The opposite faces, shown by the shaded areas in the figures is

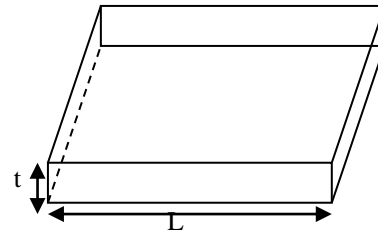- a) directly proportional to L
 b) directly proportional to t
 c) independent of L
 d) independent of t




31. When 5V potential difference is applied across a wire of length 0.1 m, the drift speed of electrons is $2.5 \times 10^{-4} \text{ ms}^{-1}$. If the electron density in the wire is $8 \times 10^{28} \text{ m}^{-3}$, the resistivity of the material is close to
 a) $1.6 \times 10^{-8} \Omega\text{m}$ b) $1.6 \times 10^{-7} \Omega\text{m}$ c) $1.6 \times 10^{-6} \Omega\text{m}$ d) $1.6 \times 10^{-5} \Omega\text{m}$
32. A wire of a certain material is stretched slowly by ten percent. Its new resistance and specific resistance become respectively.
 a) Both remain the same b) 1.1 times, 1.1 times
 c) 1.2 times 1.1 times d) 1.21 times, same
33. The resistance of an incandescent lamp is
 a) Greater when switched off
 b) Smaller when switched on
 c) Greater when switched on
 d) The same whether it is switched off or switched on
34. The graph between resistivity and temperature, for a limited range of temperatures, is a straight line for a material like
 a) Copper b) Nichrome c) Silicon d) Mercury

35. The alloys constantan and manganin are used to make standard resistance because they are
- Low resistivity
 - High resistivity
 - Low temperature coefficient of resistance
 - Both (b) and (c)
36. A block has dimensions 1 cm, 2 cm, 3 cm, Ratio of the maximum resistance to minimum resistance between any points of opposite faces of his block is
- 9 : 1
 - 1 : 9
 - 18 : 1
 - 1 : 6


37. In the circuit shown, the current in the 1Ω resistor is

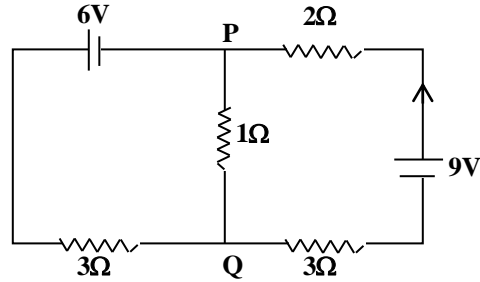- 1.3A, from P to Q
- 0A
- 0.13 A, from Q to P
- 0.13 A, from P to Q



38. In the adjoining circuit, the battery E_1 has an e.m.f of 12 volt and zero internal resistance while the battery E has an e.m.f of 2 volt. If the galvanometer G reads zero, then the value of the resistance X in ohm is

- 10
- 100
- 500
- 200

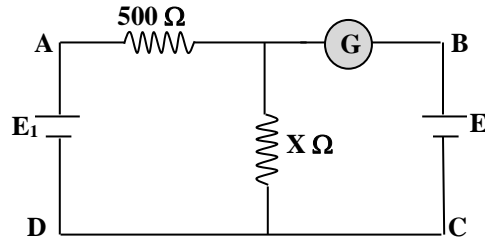


39. A student measures the terminal potential difference (V) of cell (of emf E and internal resistance r) as a function of the current (I) flowing through it. The slope, and intercept, of the graph between V and I, then, respectively, equal


- E and $-r$
- $-r$ and E
- r and $-E$
- $-E$ and r

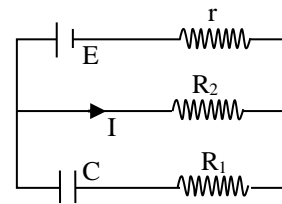40. The charge on the capacitor of capacitance C shown in the figure below will be


- CE
- $\frac{CER_1}{R_1 + r}$
- $\frac{CER_2}{R_2 + r}$
- $\frac{CER_1}{R_2 + r}$



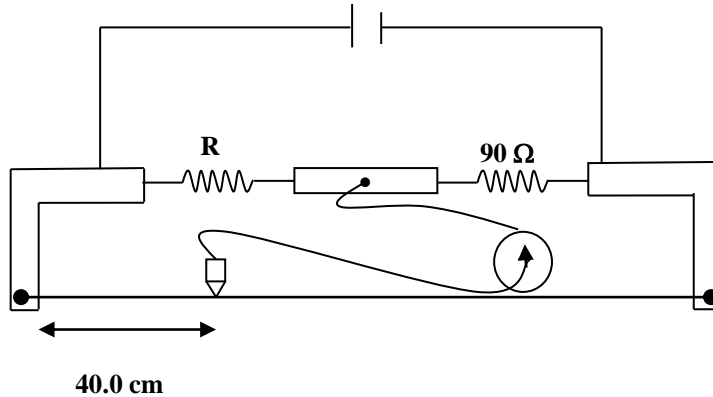41. During experiment with a metre bridge, the galvanometer shows a null point when the jockey is pressed at 40.0 cm using a standard resistance of $90\ \Omega$, as shown in the figure. The least count of the scale used in the metre bridge is 1mm. The unknown resistance is




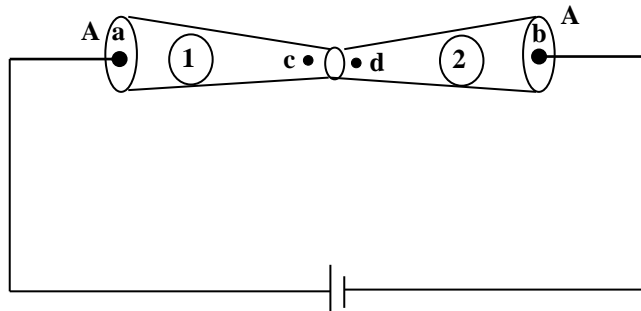- a) $60 \pm 0.15\ \Omega$ b) $135 \pm 0.56\ \Omega$ c) $60 \pm 0.25\ \Omega$ d) $135 \pm 0.23\ \Omega$
42. Two conductors (1) and (2) having non-uniform cross section are joined end to end as shown. Their areas of cross section where they join are the same. If we compare equal volumes of the two conductors, there are more electrons in conductor (1). Referring to fig, as current passes through the system of two conductors:



- a) drift speed of electrons at 'c' is less than at 'a'
 b) drift speed of electrons at 'b' is more than at 'a'
 c) drift speed of electrons at 'c' is the same as that at 'd'
 d) drift speed of electrons at 'a' is same as that at 'b'.
43. Resistance of resistor at temperature $t^\circ\text{C}$ is $R_t = R_0 (1 + \alpha t + \beta t^2)$, where R_0 is the resistance at 0°C . The temperature coefficient of resistance at temperature $t^\circ\text{C}$ is
- a) $\frac{1 + \alpha t + \beta t^2}{\alpha + 2\beta t}$ b) $(\alpha + 2\beta t)$ c) $\frac{\alpha + 2\beta t}{(1 + \alpha t + \beta t^2)}$ d) $\frac{\alpha + 2\beta t}{2(1 + \alpha t + \beta t^2)}$
44. Two cells of equal emf and of internal resistance r_1 and r_2 ($r_1 > r_2$) are connected in series. On connecting this combination to an external resistance R , it is observed that the potential difference across the first cell becomes zero. The value of R will be
- a) $r_1 + r_2$ b) $R = r_1 - r_2$ c) $\frac{r_1 + r_2}{2}$ d) $\frac{r_1 - r_2}{2}$

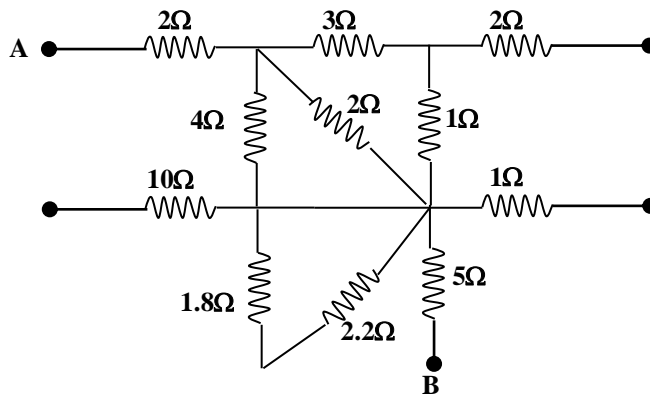45. What is the equivalent resistance between the points A and B of the network




- a) $\frac{57}{7} \Omega$ b) 8Ω c) 6Ω d) $\frac{57}{5} \Omega$

46. A copper wire and an iron wire, each having an area of cross-section A and lengths L_1 and L_2 are joined end to end. The copper end is maintained at a potential V_1 and the iron end at a lower potential V_2 . If σ_1 and σ_2 are the conductivities of copper and iron respectively, then the potential of the junction will be

- a) $\frac{\sigma_1 V_1 + \sigma_2 V_2}{(\sigma_1/L_1) + (\sigma_2/L_2)}$ b) $\frac{\frac{\sigma_1 V_1}{L_1} + \frac{\sigma_2 V_2}{L_2}}{(\sigma_1/L_1) + (\sigma_2/L_2)}$ c) $\frac{(\sigma_1/L_1) + (\sigma_2/L_2)}{\sigma_1 V_1 + \sigma_2 V_2}$ d) $\frac{\sigma_1 V_1 - \sigma_2 V_2}{(\sigma_1/L_1) - (\sigma_2/L_2)}$

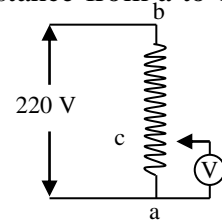47. A potential difference of 220 V is maintained across a 12000 ohm rheostat, as shown in the figure. The voltmeter has a resistance of 6000 ohm and point c at one-fourth of the distance from a to b. Therefore, the reading of the voltmeter will be



- a) 32 V
b) 36 V
c) 40 V
d) 42 V

48. Two resistances equal at 0°C with temperature coefficient of resistance α_1 and α_2 joined in series act as a single resistance in a circuit. The temperature coefficient of their single resistance will be

- a) $\alpha_1 + \alpha_2$ b) $\frac{\alpha_1 \alpha_2}{\alpha_1 + \alpha_2}$ c) $\frac{\alpha_1 - \alpha_2}{2}$ d) $\frac{\alpha_1 + \alpha_2}{2}$

49. The current density varies with radial distance r as $J = a r^2$, in a cylindrical wire of radius R. The current passing through the wire between radial distance $R/3$ and $R/2$ is

- a) $\frac{65\pi a R^4}{2592}$ b) $\frac{25\pi a R^4}{72}$ c) $\frac{65\pi a^2 R^3}{2938}$ d) $\frac{81\pi a^2 R^4}{144}$

50. In the diagram shown, all the wires have resistance R. the equivalent resistance between the upper and lower points shown in the diagram is

- a) $R/8$
b) R
c) $2R/5$
d) $3R/8$

