

II PUC – CHAPTER 03 CURRENT ELECTRICITY

Electric current

☞ Electric current = $\frac{\text{charge}}{\text{time}}$ i.e. $I = \frac{q}{t} = \frac{ne}{t}$

n – number of electrons flowing across the cross section of a conductor in time t .

☞ If a small charge dq flows in time dt then instantaneous current is $I = \frac{dq}{dt}$

☞ Current due to circular motion of charge:

Electric current $I = fq = \frac{q}{T} = \frac{qv}{2\pi r} = \frac{q\omega}{2\pi}$

f = frequency of revolution; v = velocity; r = radius of orbit; ω = angular velocity

For electron $I = fe$

Current density

☞ Current density $J = \frac{I}{A} = \sigma E = \frac{E}{\rho}$ σ = electrical conductivity; ρ = resistivity

☞ • Current through a conductor is $I = \vec{J} \cdot \vec{A} = JA \cos\theta$

• $I = \int \vec{J} \cdot d\vec{A} = \int (J \cos\theta) dA$

Drift velocity

☞ Velocity of random motion of electrons increases with increase in temperature, $v_r \propto \sqrt{T}$

☞ Relaxation time and drift velocity decreases with increase in temperature, $v_d \propto \frac{1}{\sqrt{T}}$

☞ Drift velocity of electrons $v_d = \frac{I}{nAe} = \frac{J}{ne} = \frac{\sigma E}{ne} = \frac{e\tau E}{m} = \frac{Ve\tau}{\ell m}$

where n = electron density (m^{-3}), τ - relaxation time and m – mass of electron.

E – Electric field, V – p.d across the conductor, A – area of cross section, ℓ - length of the conductor. J – Current density; σ = electrical conductivity

☞ For a wire of non-uniform cross-section $v_d \propto \frac{1}{A} \propto \frac{1}{r^2}$

Current (I) through the wire is same whereas current density (J) changes

☞ Mobility of electrons $\mu = \frac{v_d}{E} = \frac{I}{nAeE} = \frac{I\ell}{nAeV} = \frac{e\tau}{m}$

Effects of electric current

☞ Quantity of heat produced $H = I^2Rt = VIt = \frac{V^2t}{R}$ joules.

where I = current in the resistance R , t = time for which current flows

☞ If one electric heater boils a liquid in time t_1 and another heater boils the same liquid in time t_2 , then time taken by the same liquid to boil when these two heater are

(i) in series is $t = t_1 + t_2$

(ii) in parallel is $t = \frac{t_1 t_2}{t_1 + t_2}$

Ohm's Law



☞ $V \propto I$ or $V = IR$, $R =$ electrical resistance of the conductor.

☞ $R = \frac{V}{I} = \frac{W}{QI}$

☞ Conductance $G = 1/R$ (Unit: siemen (S) or mho or ohm^{-1} or A/V)

☞ For ohmic devices a plot of V vs I is a straight line

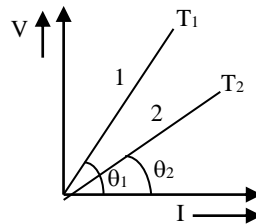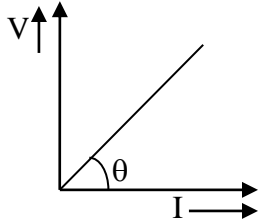
Slope = $\tan\theta = V/I =$ resistance (R)



Here $\tan \theta_1 > \tan \theta_2$
So $R_1 > R_2$
i.e. $T_1 > T_2$

☞ A plot of I Vs V is a straight line

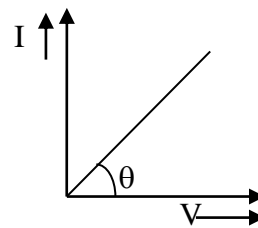Slope = $\tan\theta = I/V =$ conductance (G)



Electric power

☞ Electric power $P = \frac{W}{t} = VI = I^2R = \frac{V^2}{R}$

☞ If bulbs of different powers are joined in parallel, then bulb with highest wattage glows brighter.

☞ If bulbs of different powers are joined in series, then bulb with lowest wattage glows brighter.

☞ Effective power of the combination when devices are in series $\frac{1}{P_s} = \frac{1}{P_1} + \frac{1}{P_2} + \frac{1}{P_3}$

when applied voltage is equal to the rated voltage.

☞ Effective power of the combination when devices are in parallel $P_p = P_1 + P_2 + P_3$

when applied voltage is equal to the rated voltage.

☞ A wire fuses when square of the current (I) through it is directly proportional to the cube of its radius (r)
i.e. $I^2 \propto r^3$

Variation of resistance with its dimension:

☞ Resistance of a conductor is directly proportional to its length (L) and inversely proportional to its area of cross section (A).

☞ Resistance $R = \frac{\rho L}{A}$ where ρ is called resistivity of the material of the conductor.

☞ Resistivity of the material of the conductor, $\rho = \frac{RA}{L}$

☞ Resistivity of a cylindrical conductor $\rho = \frac{\pi r^2 R}{L} = \frac{\pi d^2 R}{4L}$

where $R =$ resistance of conductor, $A =$ area of cross-section,

$L =$ length of the conductor, $d =$ diameter of the conductor

☞ Resistivity of the material $\rho = \frac{m}{ne^2\tau}$


where $m =$ mass of the electron, $e =$ charge of the electron, $n =$ number density of electrons, $\tau =$ relaxation time

☞ The reciprocal of resistivity is called conductivity $\sigma = 1/\rho$


Also $\sigma = J/E$ where J – current density and E electric field between the ends of the conductor.

Resistance of different shaped conductors

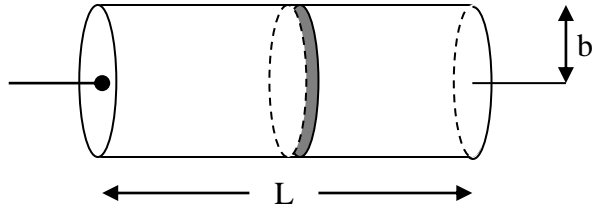Resistance of solid or hollow cylindrical wire




$$R = \frac{\rho L}{\pi b^2}$$

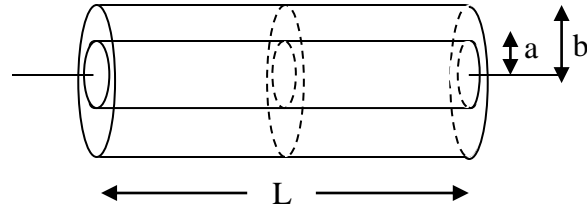

$$R = \frac{\rho L}{\pi (b^2 - a^2)}$$

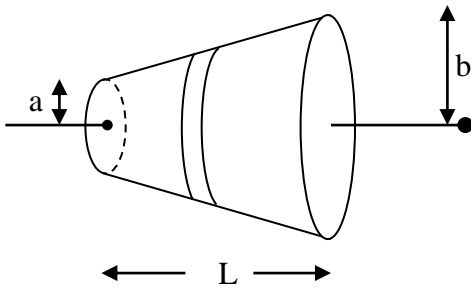Resistance of a wire of non-uniform area of cross section



$$R = \frac{\rho L}{\pi ab}$$

(Here, $(b - a) \ll L$)

Resistance of stretched wire

- When a wire is stretched $R_2 = R_1 \left(\frac{\ell_2}{\ell_1} \right)^2 = R_1 \left(\frac{A_1}{A_2} \right)^2 = R_1 \left(\frac{r_1}{r_2} \right)^4$ i.e. $R \propto \ell^2 \propto \frac{1}{A^2} \propto \frac{1}{r^4}$

ℓ_1 and ℓ_2 are the initial and final lengths.

A_1 and A_2 are the initial and final area of cross section.

r_1 and r_2 is the initial and final radius.

- If the length of metallic wire becomes n times, its resistance becomes n^2 times.
- If the radius of metallic wire becomes n times, its resistance becomes $\frac{1}{n^4}$ times.
- If the area of cross section of the metallic wire becomes n times, then its resistance becomes $1/n^2$ times.

Variation of resistance of a conductor with temperature

The electrical resistance of most of the metallic conductors increases with increase in temperature according to $R_t = R_0 (1 + \alpha t)$

R_t = resistance of conductor at temperature $t^\circ\text{C}$ and R_0 = resistance of conductor at temperature 0°C

α is called the temperature coefficient of resistance of the material of the conductor.


TCR of conductor is $\alpha = \frac{R_t - R_0}{R_0 t} = \frac{R_2 - R_1}{R_1 t_2 - R_2 t_1}$

R_1 is resistance of conductor at $t_1^\circ\text{C}$, R_2 is resistance of conductor at $t_2^\circ\text{C}$

Also $\alpha \approx \frac{R_2 - R_1}{R_1(t_2 - t_1)} = \frac{\Delta R}{R_1 \Delta t}$

☞ A plot of R_t Vs temperature of a conductor is a straight line whose slope is $R_0\alpha$ and y-intercept is R_0 .

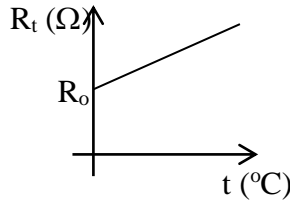Also $\alpha = \frac{\text{slope}}{\text{Y - int ercept}}$




☞ Variation of resistivity of a conductor with temperature $\rho_t = \rho_0 (1 + \alpha t)$
 ρ_t = Resistivity at $t^\circ\text{C}$, ρ_0 = Resistivity at 0°C .
 α = temperature coefficient of resistivity of the conductor.

Simple circuit

☞ Emf of the cell $E = I(R + r)$

☞ Current in the circuit $I = \frac{E}{R + r}$

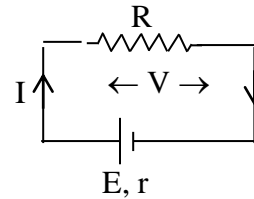R = resistance of the external circuit
 r = internal resistance of the cell.



☞ Terminal P.d $V = IR = \frac{ER}{R + r} = E - Ir$

☞ P.d across the internal resistance $V' = Ir$

☞ Power dissipated in external resistance $P = VI = I^2R = \left(\frac{E}{R + r}\right)^2 R$

☞ Power dissipated is maximum when $R = r$

$$P_{\max} = \frac{E^2}{4R}$$

☞ Also $V = E$ when $r \approx 0$ or $R = \infty$

The emf of a cell is equal to the potential difference between the terminals of the cell, when the cell is in open circuit. i.e. when the current drawn from the cell is zero.

☞ When a cell is being charged, the current is given to the cell and the p.d across its terminal is always greater than its emf i.e. $V = E + Ir$ ($E < V$)

Potentiometer

☞ Potential gradient in a potentiometer $x = \frac{ER}{(R + r)L}$ (V/m)

E – emf of the primary or standard cell, L - length of potentiometer wire,
 R – resistance of potentiometer wire, r – resistance of the standard cell.


☞ Internal resistance of a cell, $r = R\left(\frac{L - \ell}{\ell}\right)$ where L is the balancing length for the given cell in open circuit

and ℓ is the balancing length for the same cell in closed circuit.

☞ **Comparisons of two cells:**


Ratio of emfs of two cells $\frac{E_1}{E_2} = \frac{\ell_1}{\ell_2}$

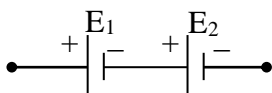ℓ_1 and ℓ_2 are balancing lengths for given cells.



$$(E_1 + E_2) = x \ell_1$$
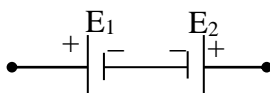
$$\frac{E_1 + E_2}{E_1 - E_2} = \frac{\ell_1}{\ell_2} \text{ or}$$





$$(E_1 - E_2) = x \ell_2$$

$$\frac{E_1}{E_2} = \frac{\ell_1 + \ell_2}{\ell_1 - \ell_2}$$

☞ Emf of the secondary cell = potential gradient \times balancing length.

Series or parallel combination of resistances

1)

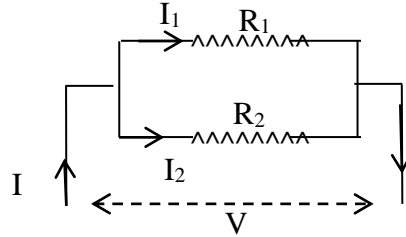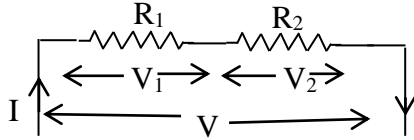


Series	Parallel
Current through each resistance is same	P.d across each resistance is same
P.d across the combination $V = V_1 + V_2$ $V_1 = \frac{VR_1}{R_1 + R_2}$ and $V_2 = \frac{VR_2}{R_1 + R_2}$	Main current $I = I_1 + I_2$ $I_1 = \frac{IR_2}{R_1 + R_2}$ and $I_2 = \frac{IR_1}{R_1 + R_2}$
Effective resistance $R_S = R_1 + R_2 + R_3 + \dots + R_n$	Effective resistance $\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$
Effective resistance is always greater than highest value of resistance	Effective resistance is always less than least value of resistance
For two resistors $R_S = R_1 + R_2$	For two resistors $R_P = \frac{R_1 R_2}{R_1 + R_2}$
For n identical resistors $R_S = nR$ $V_1 = V_2 = V_3 \dots = V/n$	For n identical resistors $R_P = R/n$ $I_1 = I_2 = I_3 \dots = I/n$
Effective conductance $\frac{1}{G_S} = \frac{1}{G_1} + \frac{1}{G_2} + \frac{1}{G_3} + \dots + \frac{1}{G_n}$	Effective conductance $G_P = G_1 + G_2 + G_3 + \dots + G_n$
P.d across each resistor $V \propto R$ $V_1 : V_2 : V_3 = R_1 : R_2 : R_3$	Current through each resistor $I \propto \frac{1}{R}$ $I_1 : I_2 : I_3 = \frac{1}{R_1} : \frac{1}{R_2} : \frac{1}{R_3}$
Power dissipated in each resistor $P \propto R$	Power dissipated in each resistor $P \propto \frac{1}{R}$


☞ Ratio of effective resistance of n identical resistors first connected in series and then in parallel $R_S/R_P = n^2$

☞ Twelve identical wires each of resistance R are joined to form a cube. Then equivalent resistance between

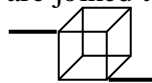
a) the ends of a face diagonal = $\frac{3R}{4}$



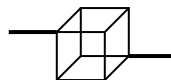b) diagonally opposite corners = $\frac{5R}{6}$



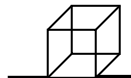c) any two adjacent corners = $\frac{7R}{12}$



Branch currents

☞ When two resistances are connected in parallel,
 Branch current = $\frac{\text{Main current} \times \text{resistance of other branch}}{\text{sum of the resistance}}$

i.e. $I_1 = \frac{IR_2}{R_1 + R_2}$ or $I_2 = \frac{IR_1}{R_1 + R_2}$

☞ When resistances are connected in parallel branch current is also given by

$I_1 = \frac{IR_P}{R_1}$ or $I_2 = \frac{IR_P}{R_2}$ where R_P is the effective resistance in parallel and I is the main current.

☞ When n identical resistances are connected in parallel then

Branch current = $\frac{\text{Main Current}}{\text{Number of branches}}$

Combination of cells

1)

Series	Parallel
Cells are said to be in series such that negative terminal of a cell is connected to the positive terminal of the other cell and so on.	Cells are said to be in parallel if all negative terminals of the cells are connected together to one terminal and all positive terminals are connected to the other terminal.
Current through each cells is same	P.d across each cells is same
$V = V_1 + V_2 + V_3, \dots$ $V_1 = E_1 - Ir_1; V_2 = E_2 - Ir_2$	$I = I_1 + I_2 + I_3, \dots$ $I_1 = \frac{E_1 - V}{r_1}; I_2 = \frac{E_2 - V}{r_2}$
Equivalent internal resistance $r_{eq} = r_1 + r_2 + r_3 + \dots$	Equivalent internal resistance $\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots$
Equivalent emf $E_{eq} = E_1 + E_2 + E_3 + \dots$	$\frac{E_{eq}}{r_{eq}} = \frac{E_1}{r_1} + \frac{E_2}{r_2} + \frac{E_3}{r_3} + \dots$
Current through the circuit $I = \frac{E_{eq}}{R + r_{eq}}$	Current through the circuit $I = \frac{E_{eq}}{R + r_{eq}}$
Terminal p.d $V = E_{eq} - I r_{eq}$	Terminal p.d $V = E_{eq} - I r_{eq}$

2) Combination of identical cells


For n identical cells in series	For m identical cells in parallel
Equivalent emf $E_{eq} = nE$	Equivalent emf $E_{eq} = E$ (same as that of one cell)
Equivalent internal resistance $r_{eq} = nr$	Equivalent internal resistance $r_{eq} = r/m$
Current through the circuit $I = \frac{nE}{R + nr}$	Current through the circuit is $I = \frac{mE}{mR + r}$
Terminal p.d $V = E_{eq} - I r_{eq}$	Terminal p.d $V = E_{eq} - I r_{eq}$
P.d across each cell $V' = V/n$	Current through each cell $I' = I/m$
Current is maximum if $R \gg nr$	Current is maximum if $r \gg mR$
$I_{max} = \frac{nE}{R}$	$I_{max} = \frac{mE}{r}$

- In series combination of n identical cells if N cells are oppositely connected then net emf of the circuit is $E' = (n - 2N)E$ where E – Emf of each cell.


☞ If two cells of emfs E_1 and E_2 and internal resistances r_1 and r_2 are connected in parallel to an external resistance R

- Effective internal resistance $r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$
- Effective emf $E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$
- Current through external resistance, $I = \frac{E_{eq}}{R + r_{eq}}$
- If cells are connected with opposite polarity
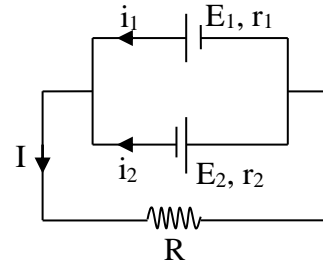
$$\text{Effective emf } E_{eq} = \frac{E_1 r_2 - E_2 r_1}{r_1 + r_2}$$



☞ Mixed grouping:

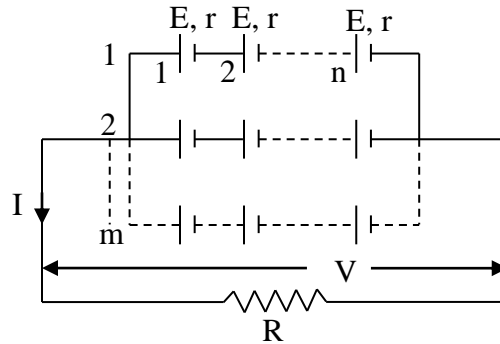

n = number of cells in each row; m = number of rows
Total number of cells = mn

- Equivalent emf of the combination $E_{eq} = nE$
- Equivalent internal resistance $r_{eq} = \frac{nr}{m}$
- Main current $I = \frac{mnE}{mR + nr}$
- Current through the circuit is maximum if external resistance is equal to the total internal resistance of the cells. i.e. $R = \frac{nr}{m}$


$$\text{Maximum current is } I_{max} = \frac{mE}{2r} = \frac{nE}{2R} = \frac{mnE}{2\sqrt{mnrR}}$$

Wheatstone's network

- ☞ The condition for electrical balance being $\frac{P}{Q} = \frac{R}{S}$
- ☞ Balanced condition is independent of galvanometer resistance, emf of the cell and its internal resistance.

☞ In a balanced Wheatstone's network,


- Current through the galvanometer $I_g = 0$
- P.d across galvanometer $V_g = 0$
- Ratio of adjacent resistances is equal. i.e. $\frac{P}{Q} = \frac{R}{S}$ or $PS = QR$
- Current through P & Q is equal. Also current through R and S are equal
- P.d across P = P.d across R and P.d across Q = p.d across S
- Effective external resistance of the circuit $R_{eff} = \frac{(P + Q)(R + S)}{P + Q + R + S}$
- When all the four resistances are identical then $R_{eff} = R$

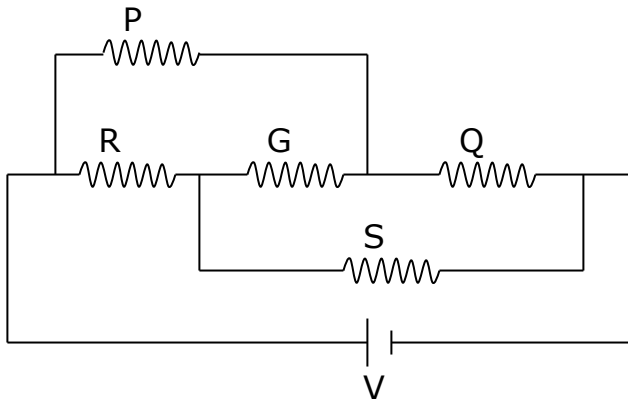


Above circuit is equivalent to Wheatstones network.

Equivalent resistance of unbalanced network:
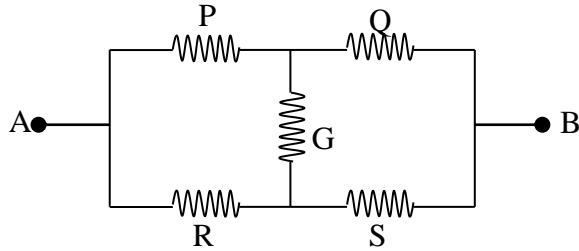
$$R_{AB} = \frac{(P+Q)RS + PQ(R+S) + (P+Q)(R+S)G}{(P+Q+R+S)G + (P+R)(Q+S)}$$


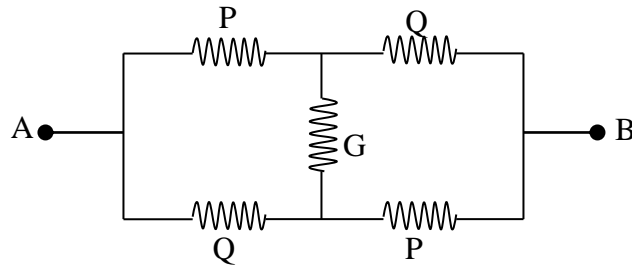
$$R_{AB} = \frac{2PQ + (P+Q)G}{2G + P + Q}$$



Metre Bridge

If P is the unknown resistance in the left gap, Q is the known resistance in the right gap. L is the balancing length (in m). Then $P = \frac{QL}{1-L} \Omega$

If L is in cm then $P = \frac{QL}{100-L}$

When $P = Q$, then balancing length $L = 0.5 \text{ m}$ or 50 cm .